

Smart Multimeter Using Microcontroller Systems — Assignment 1 (Ayush Muttepawar 240243)

Task A

1. Purpose:

A voltage divider is used to reduce a high voltage to a lower, safe voltage that a device can measure.

In measurement systems like a digital multimeter or Arduino, the input voltage is divided so it does not damage the ADC pin.



2. ADC reading-to-voltage conversion formula:

$$V_{out} = V_{in} * R2 / (R1 + R2)$$

$$\text{Voltage} = \text{ADC Value} * V_{ref} / 1023$$

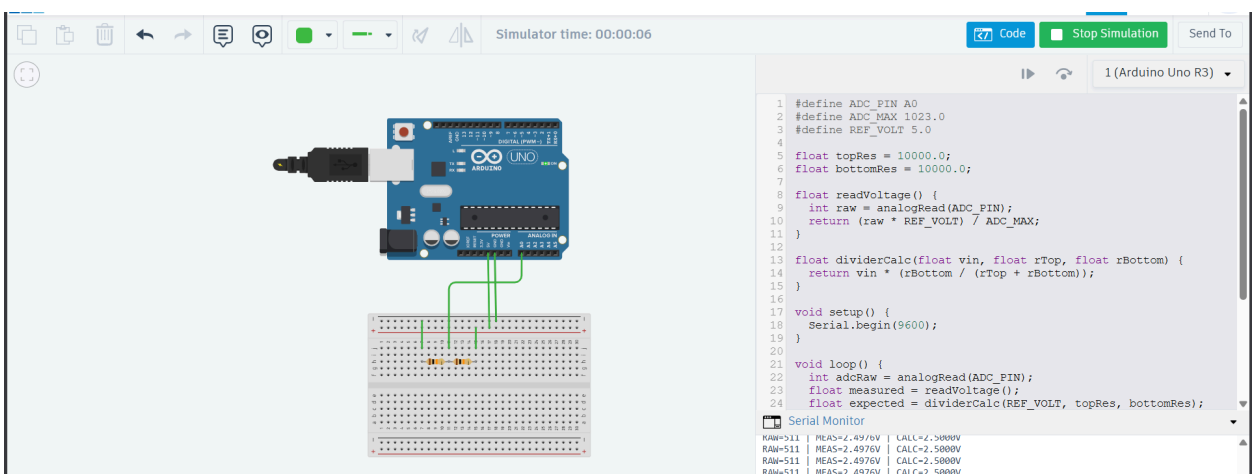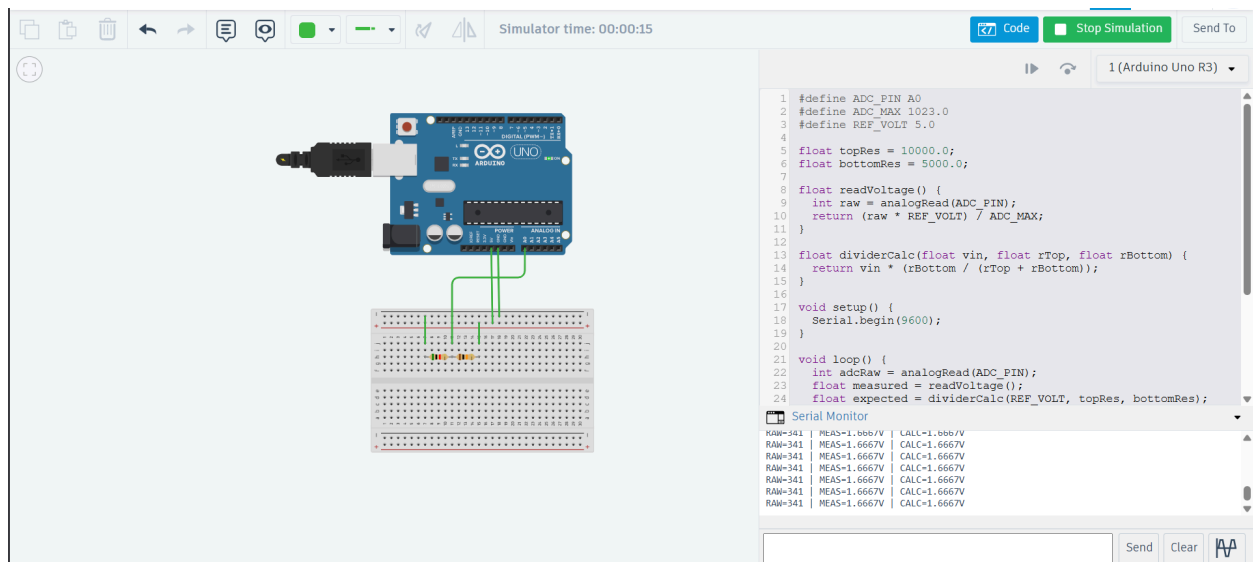
3. Observations: error, noise, or unexpected results:

Measured voltages were close to theoretical values for all resistor combinations and small errors occurred due to ADC resolution and resistor tolerances.



Smart Multimeter Using Microcontroller Systems —

Assignment 1 (Ayush Muttepawar 240243)

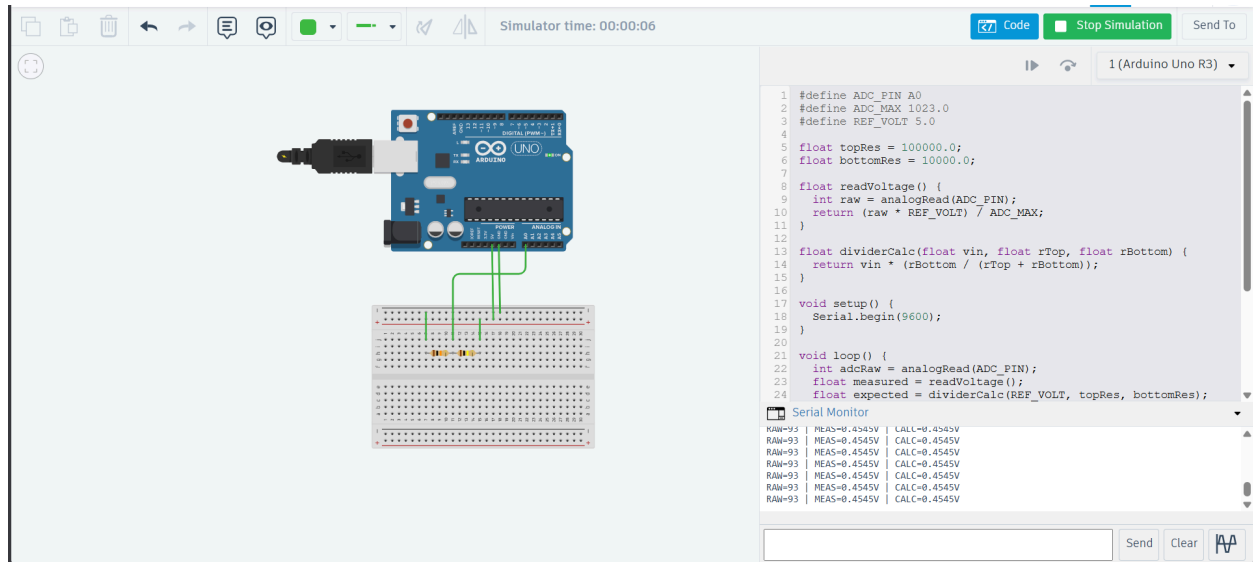

R1	R2	Theoretical Vout	Measured Vout
10k	5k	1.6667	1.6667
10k	10k	2.5000	2.4976
100k	10k	0.4545	0.4545

4. Code:

```
#define ADC_PIN A0
#define ADC_MAX 1023.0
#define REF_VOLT 5.0
```

```
float topRes = 100000.0;
float bottomRes = 10000.0;
```

```
float readVoltage() {
  int raw = analogRead(ADC_PIN);
  return (raw * REF_VOLT) / ADC_MAX;
}
```

```
float dividerCalc(float vin, float rTop, float rBottom) {
```

Smart Multimeter Using Microcontroller Systems —


Assignment 1 (Ayush Muttepawar 240243)

```
    return vin * (rBottom / (rTop + rBottom));  
}  
  
void setup() {  
    Serial.begin(9600);  
}  
  
void loop() {  
    int adcRaw = analogRead(ADC_PIN);  
    float measured = readVoltage();  
    float expected = dividerCalc(REF_VOLT, topRes, bottomRes);  
  
    Serial.print("RAW=");  
    Serial.print(adcRaw);  
    Serial.print(" | MEAS=");  
    Serial.print(measured, 4);  
    Serial.print("V | CALC=");  
    Serial.print(expected, 4);  
    Serial.println("V");  
  
    delay(600);  
}
```

Smart Multimeter Using Microcontroller Systems — Assignment 1 (Ayush Muttepawar 240243)

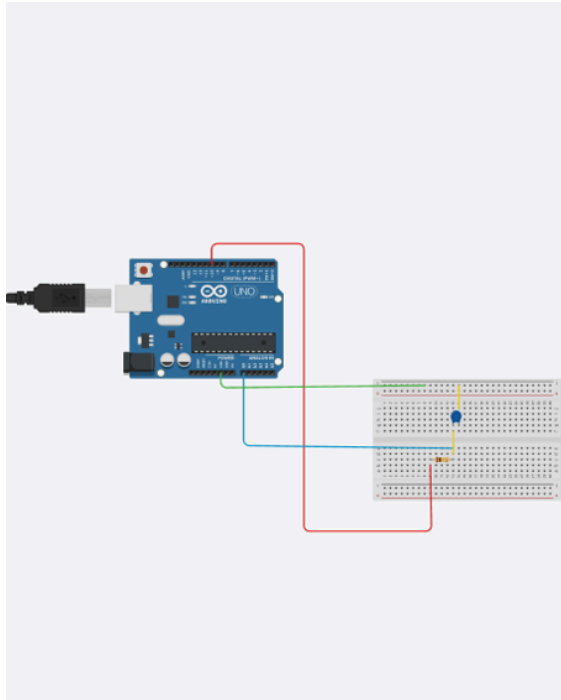Task B


Smart Multimeter Using Microcontroller Systems — Assignment 1 (Ayush Muttepawar 240243)



```
19 }
20
21 void loop() {
22
23     // Discharge the capacitor completely
24     digitalWrite(chargePin, LOW);
25     delay(50); // ensure full discharge
26
27     // Calculate ADC threshold for 63% voltage
28     int adcLimit = (int)(thresholdRatio * 1023.0);
29
30     // Begin charging the capacitor
31     digitalWrite(chargePin, HIGH);
32
33     // Start timing
34     unsigned long startTime = micros();
35
36     int adcReading = 0;
37     while (adcReading < adcLimit) {
38         adcReading = analogRead(sensePin);
39     }
40
41     unsigned long stopTime = micros();
42     unsigned long elapsedTime = stopTime - startTime; // in microseconds
43
44     float capacitance = (float)elapsedTime / resistorValue;
45
46     Serial.print("Time to reach 63%: ");
47     Serial.print(elapsedTime);
48     Serial.print(" us | Estimated Capacitance: ");
49     Serial.print(capacitance);
50     Serial.println(" uF");
51 }
```

Serial Monitor

Time to reach 63%	Estimated Capacitance
19944 us	1.99 uF
18232 us	1.82 uF
18220 us	1.82 uF
18224 us	1.82 uF
18224 us	1.82 uF
18228 us	1.82 uF
18228 us	1.82 uF

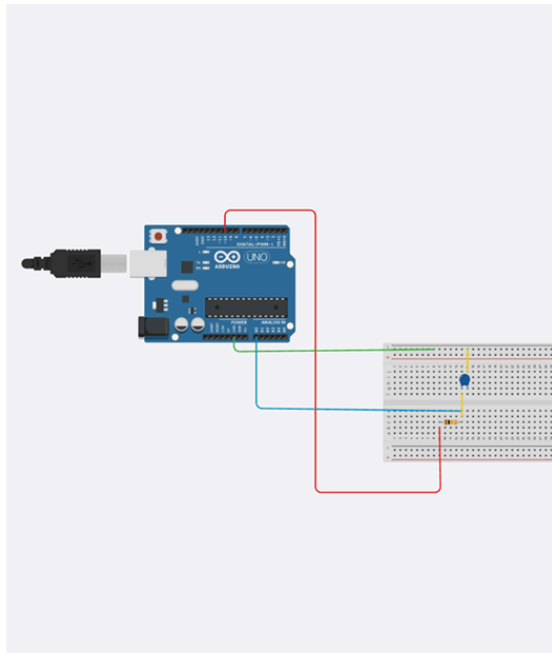

```
19 }
20
21 void loop() {
22
23     // Discharge the capacitor completely
24     digitalWrite(chargePin, LOW);
25     delay(50); // ensure full discharge
26
27     // Calculate ADC threshold for 63% voltage
28     int adcLimit = (int)(thresholdRatio * 1023.0);
29
30     // Begin charging the capacitor
31     digitalWrite(chargePin, HIGH);
32
33     // Start timing
34     unsigned long startTime = micros();
35
36     int adcReading = 0;
37     while (adcReading < adcLimit) {
38         adcReading = analogRead(sensePin);
39     }
40
41     unsigned long stopTime = micros();
42     unsigned long elapsedTime = stopTime - startTime; // in microseconds
43
44     float capacitance = (float)elapsedTime / resistorValue;
45
46     Serial.print("Time to reach 63%: ");
47     Serial.print(elapsedTime);
48     Serial.print(" us | Estimated Capacitance: ");
49     Serial.print(capacitance);
50     Serial.println(" uF");
51 }
```

Serial Monitor

Time to reach 63%	Estimated Capacitance
9972 us	1.00 uF
9988 us	0.99 uF
9988 us	0.99 uF
9988 us	0.99 uF
9920 us	0.99 uF
9904 us	0.99 uF
9916 us	0.99 uF

1. RC Time Constant and 63% Significance


The RC time constant (τ) is the time taken by a capacitor to charge to about 63% of the supply voltage through a resistor. This happens because of the exponential charging behavior of capacitors. At one time constant, the voltage across the capacitor reaches $0.63 \times V_{\square}$, which makes it a reliable point for measuring capacitance using time.

Smart Multimeter Using Microcontroller Systems —

Assignment 1 (Ayush Muttepawar 240243)

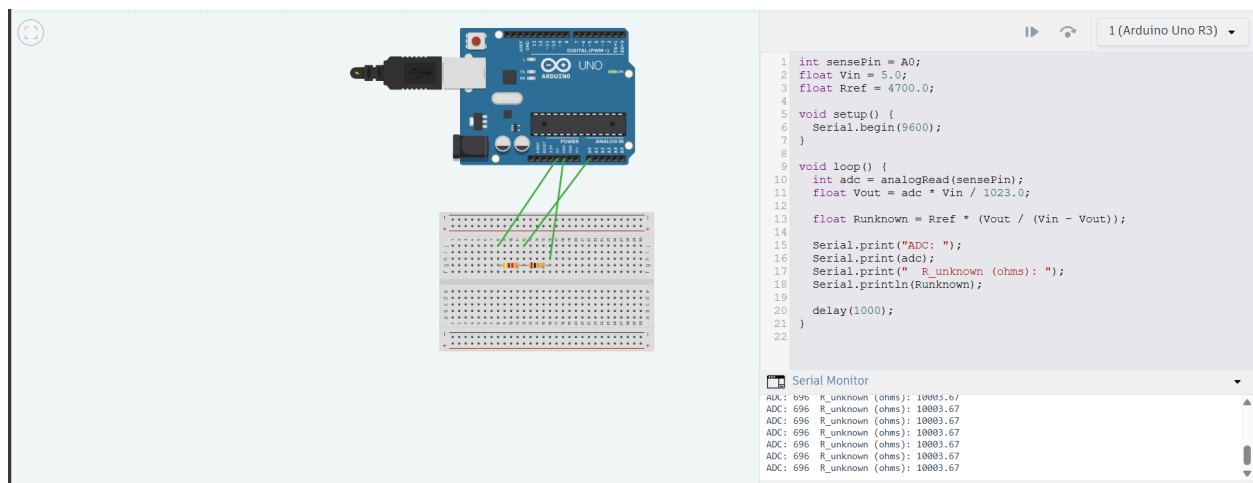
2. Sources of Error

Measurement errors occur due to resistor and capacitor tolerance, Arduino ADC resolution, electrical noise, and timing delays in the microcontroller. Simulation limitations in Tinkercad can also cause small deviations.



Smart Multimeter Using Microcontroller Systems —

Assignment 1 (Ayush Muttepawar 240243)

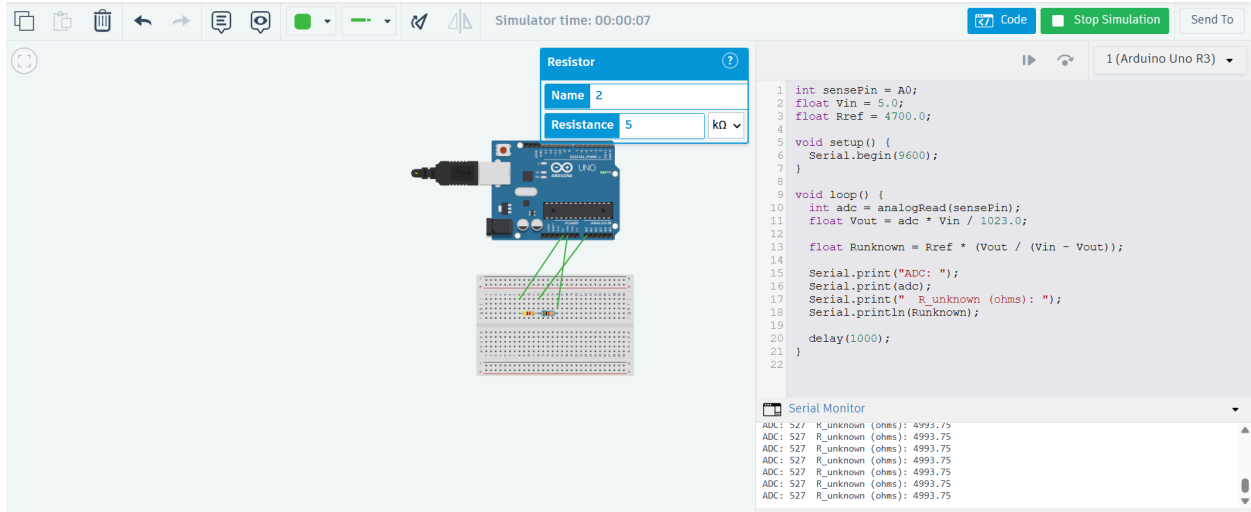

Simulator time: 00:00:07

Resistor


Name 2

Resistance 5 kΩ

```
1 int sensePin = A0;
2 float Vin = 5.0;
3 float Rref = 4700.0;
4
5 void setup() {
6   Serial.begin(9600);
7 }
8
9 void loop() {
10  int adc = analogRead(sensePin);
11  float Vout = adc * Vin / 1023.0;
12
13  float Runknown = Rref * (Vout / (Vin - Vout));
14
15  Serial.print("ADC: ");
16  Serial.print(adc);
17  Serial.print(" R_unknown (ohms): ");
18  Serial.println(Runknown);
19
20  delay(1000);
21 }
22
```

Serial Monitor

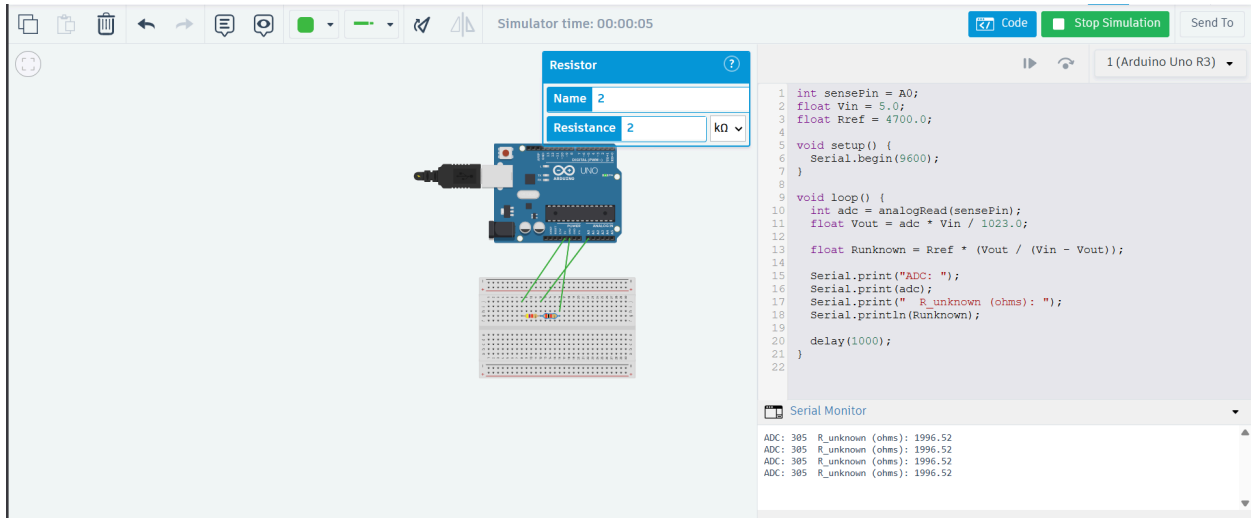ADC: 527 R_unknown (ohms): 4993.75
ADC: 527 R_unknown (ohms): 4993.75
ADC: 527 R_unknown (ohms): 4993.75
ADC: 527 R_unknown (ohms): 4993.75
ADC: 527 R_unknown (ohms): 4993.75
ADC: 527 R_unknown (ohms): 4993.75



Simulator time: 00:00:05

Resistor

Name 2

Resistance 2 kΩ

```
1 int sensePin = A0;
2 float Vin = 5.0;
3 float Rref = 4700.0;
4
5 void setup() {
6   Serial.begin(9600);
7 }
8
9 void loop() {
10  int adc = analogRead(sensePin);
11  float Vout = adc * Vin / 1023.0;
12
13  float Runknown = Rref * (Vout / (Vin - Vout));
14
15  Serial.print("ADC: ");
16  Serial.print(adc);
17  Serial.print(" R_unknown (ohms): ");
18  Serial.println(Runknown);
19
20  delay(1000);
21 }
22
```

Serial Monitor

ADC: 385 R_unknown (ohms): 1996.52
ADC: 385 R_unknown (ohms): 1996.52
ADC: 385 R_unknown (ohms): 1996.52
ADC: 385 R_unknown (ohms): 1996.52